

Circuits Puzzles: Scoring Rubric

SK Partners

(Rubric last updated August 24, 2016)

Miscellaneous Notes

99 vs. 0:

- Blank ballots are scored 99. Blank ballots include:
 - Ballots with nothing written on them.
 - Ballots with only student names or ID numbers.
- If a ballot has anything written/drawn on it that is related to the puzzles or circuits, continue to score that entire puzzle using the rubrics below, i.e., give 0s where applicable.

Batteries in circuits:

- In the rubrics below, it is assumed that drawings of batteries in circuits should show wires connecting to *opposite* ends of the battery (not, for example, wires connected to only one end of the battery).

Puzzle 1: Light the Bulb

Part 1 of 1: “Draw a picture of your circuit!”

- Possible score points: 1 or 0
- **1 point** requires a drawing that shows:
 - All circuit components--battery, light bulb, and connecting wires; AND
 - The circuit is closed.
 - Note: Circuits may have multiple bulbs and/or batteries.
- **0 points** if:
 - No circuit is drawn;
 - Circuit is open; OR
 - Circuit is missing the battery, bulb, or connecting wires.

Maximum Total Points Possible: 1

Puzzle 2: Pink “?” Box

Part 1 of 2 (box contents): “What’s inside the pink box?”

- Possible score points: 1 or 0
- **1 point** requires response of “wire” [the answer is circled or otherwise clearly indicated]
 - **NOTE:** Box contents may be shown in the ballot’s top section (circle your answer) and/or in the ballot’s bottom section (in circuit drawing).
- **0 points** if no response, battery is circled, or something other than wire is clearly indicated in some way

Part 2 of 2 (circuit drawing): “Draw a picture of the circuit that told you what’s inside the pink box.”

- Possible score points: 1 or 0
- **1 point** requires a drawing that shows:
 - Closed circuit, with just the pink box and a bulb; OR
 - Closed circuit, with the pink box, a bulb, and a battery.
- **0 points** if:
 - No circuit is drawn;
 - Circuit is open;
 - Drawing is only of the box’s contents; OR
 - Circuit is closed and includes only the pink box and a battery (but no bulb).

RULES FOR CALCULATING TOTAL SCORES:

- **Option A: Sum of scores.** Sum (a) score for box contents and (b) score for circuit drawing.
 - Maximum possible points = 2
- **Option B: 1/0 scoring.**
 - If contents score = 1 AND drawing score = 1, then total score = 1.
 - If contents score = 0 OR drawing score = 0, then total score = 0.
 - Maximum possible points = 1.

Puzzle 3: Electric Mystery Mania (3 boxes)

<p>Part 1 of 2 (Box Contents): “What’s inside the box?”</p> <p>Possible score points: 1 or 0</p> <p>NOTE: Box contents may be provided in the ballot’s top section (circle your answer) and/or in the ballot’s bottom section (circuit drawing).</p>	<p>Part 2 of 2 (Circuit Drawing): “Draw a picture of the circuit that told you what’s inside the box.”</p> <p>Possible score points: 1 or 0</p>
RED BOX	
<p>1 point requires response of “WIRE” [the answer is circled or clearly indicated in some other way]</p> <p>0 points if no response, something else is circled, or something else is clearly indicated in some way</p>	<p>1 point requires a drawing that shows:</p> <ul style="list-style-type: none"> • Closed circuit with <ul style="list-style-type: none"> ○ The box, ○ A bulb, and ○ A battery. <p>0 points if:</p> <ul style="list-style-type: none"> • No circuit is drawn; • Circuit is open; • Drawing is only of the box’s contents; OR • Circuit is closed but with incorrect components.
BLUE BOX	
<p>1 point requires response of “BULB” [the answer is circled or clearly indicated in some other way]</p> <p>0 points if no response, something else is circled, or something else is clearly indicated in some way</p>	<p>1 point requires a drawing that shows:</p> <ul style="list-style-type: none"> • Closed circuit with <ul style="list-style-type: none"> ○ The box, ○ A bulb, and ○ A battery. <p>0 points if:</p> <ul style="list-style-type: none"> • No circuit is drawn; • Circuit is open; • Drawing is only of the box’s contents; OR • Circuit is closed but with incorrect components.
YELLOW BOX	
<p>1 point requires response of “2 BATTERIES” or “BATTERY” [the answer is circled or clearly indicated in some other way]</p> <p>0 points if no response, something else is circled, or something else is clearly indicated in some way</p>	<p>1 point requires a drawing that shows:</p> <ul style="list-style-type: none"> • Closed circuit with <ul style="list-style-type: none"> ○ The box, and ○ A bulb. <p>0 points if:</p> <ul style="list-style-type: none"> • No circuit is drawn; • Circuit is open; • Drawing is only of the box’s contents; OR • Circuit is closed but with incorrect components.

RULES FOR CALCULATING TOTAL SCORES (FOR EACH BOX):

- ***Option A: Sum of scores.*** *Sum (a) score for box contents and (b) score for circuit drawing.*
 - *Maximum possible points = 2*
- ***Option B: 1/0 scoring.***
 - *If contents score = 1 AND drawing score = 1, then total score = 1.*
 - *If contents score = 0 OR drawing score = 0, then total score = 0.*
 - *Maximum possible points = 1.*

Puzzle 4: Motor





Part 1 of 2 (battery direction): “Which way is the battery facing?”

- Possible score points: 1 or 0
- **1 point** requires correct battery orientation
 - LEFT side of box: +
 - RIGHT side of box: -
 - NOTE: Battery direction may be shown in the ballot’s top section (using the answer spaces provided) and/or *in the ballot’s bottom section (in circuit drawing)*.
- **0 points** if:
 - No answer is provided; OR
 - + or - are marked on the wrong sides of the mystery box; OR
 - “L” and/or “R” are written in the answer spaces provided.

Part 2 of 2 (circuit drawing): “Draw pictures of the circuits that told you which way the battery is facing.”

- Possible score points: 0-2 (partial credit possible)
- There are two possible solution strategies, each of which is scored differently and elaborated below: (i) compare two circuits, or (ii) reverse polarity of batteries in series.

i. "Compare two circuits" solution strategy

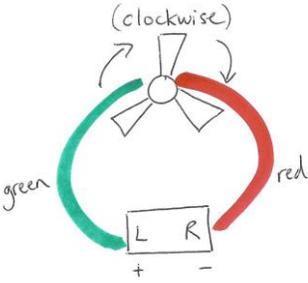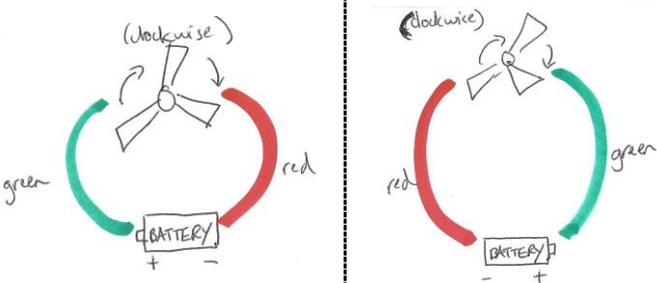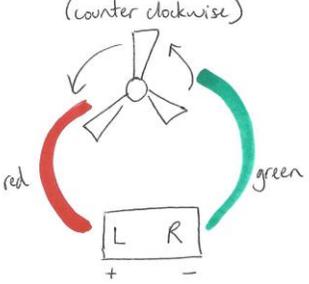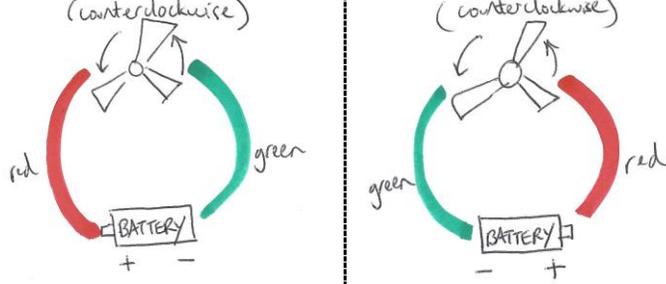Circuit 1: BOX and Motor (with fan)	Circuit 2: BATTERY and Motor (with fan)
<p>1 point requires a drawing that shows:</p> <ul style="list-style-type: none"> • Closed circuit with <ul style="list-style-type: none"> ○ The box, and ○ The motor/fan. • Complete and correct labels: <ul style="list-style-type: none"> ○ Correct direction of the fan, and ○ Colors of the wires (red and green). <p>0.5 points requires a drawing that shows:</p> <ul style="list-style-type: none"> • Closed circuit with <ul style="list-style-type: none"> ○ The box, and ○ The motor/fan. • Labels on drawing are missing, incorrect, or incomplete. <p>0 points if:</p> <ul style="list-style-type: none"> • This circuit is not drawn; OR • Circuit is open. 	<p>1 point requires a drawing that shows:</p> <ul style="list-style-type: none"> • Closed circuit with <ul style="list-style-type: none"> ○ The battery, and ○ The motor/fan. • Complete and correct labels: <ul style="list-style-type: none"> ○ + and - sides of the battery, ○ Correct direction of the fan, and ○ Colors of the wires (red and green). <p>0.5 points requires a drawing that shows:</p> <ul style="list-style-type: none"> • Closed circuit with <ul style="list-style-type: none"> ○ The battery, and ○ The motor/fan. • Labels on drawing are missing, incorrect, or incomplete. <p>0 points if:</p> <ul style="list-style-type: none"> • This circuit is not drawn; OR • Circuit is open.
<p>Examples of Correct Drawings:</p> 	<p>Examples of Correct Drawings:</p> 
	
<p>TOTAL POINTS for Circuit DRAWING: Add up ALL points from above.</p>	

RULES FOR CALCULATING TOTAL SCORES:

- ***Option A: Sum of scores.*** *Sum (a) score for motor direction and (b) score for motor circuit drawing(s).*
 - *Maximum possible points = 3*
 - *Possible score points: 0, 0.5, 1.0, 1.5, 2.0, 2.5, 3.0.*
- ***Option B: 1/0 scoring.***
 - *If direction score = 0 OR drawing score = 0, then total score = 0.*
 - *If direction score = 1 AND drawing score > 0, then total score = sum of scores.*
 - *Maximum possible points = 3*
 - *Possible score points: 0, 1.0, 1.5, 2.0, 2.5, 3.0.*

ii. “Reverse polarity of batteries in series” solution strategy

2 points requires a drawing that shows:

- Closed circuit with
 - The box,
 - The battery, and
 - The motor/fan.
- Both of the following required labels:
 - Direction of the battery (+ and - sides clearly marked), AND
 - Correct indication of whether the fan turns in the circuit drawn:
 - Fan *turns* if both batteries are correctly in series (+ connected to -)
 - Fan *does not turn* with reverse polarity (+ connected to +, or - connected to -)

1.25 points requires a drawing that shows:

- Closed circuit with
 - The box,
 - The battery, and
 - The motor/fan.
- One but not both of the following required labels:
 - Direction of the battery (+ and - sides clearly marked), OR
 - Correct indication of whether the fan turns in the circuit drawn:
 - Fan *turns* if both batteries are correctly in series (+ connected to -)
 - Fan *does not turn* with reverse polarity (+ connected to +, or - connected to -)

0.5 points requires a drawing that shows:

- Closed circuit with
 - The box,
 - The battery, and
 - The motor/fan.
- Both labels on drawing (battery direction, whether fan turns) are missing or incorrect.

0 points if:

- No circuit drawn; OR
- Circuit is open.

RULES FOR CALCULATING TOTAL SCORES:

- ***Option A: Sum of scores.*** Sum (a) score for motor direction and (b) score for motor circuit drawing(s).
 - *Maximum possible points = 3*
 - *Possible score points: 0, 0.5, 1.25, 1.5, 2.0, 2.25, 3.0.*
- ***Option B: 1/0 scoring.***
 - *If direction score = 0 OR drawing score = 0, then total score = 0.*
 - *If direction score = 1 AND drawing score > 0, then total score = sum of scores.*
 - *Maximum possible points = 3.*
 - *Possible score points: 0, 1.0, 1.5, 2.25, 3.0.*